

Supporting Multiple SD Devices with CPLDs

Creating an SD multiplexer using CPLDs.



by Mark Ng
Staff Applications Engineer, CPLD Applications Engineering
Xilinx, Inc.
mark.ng@xilinx.com

There has been an increasing demand to add multiple Secure Digital (SD) devices in a single system. The problem, however, is that most host devices/processors – for example Intel PXA270, TI OMAP, or Qualcomm MSM processors – only provide a single SD interface. Fortunately, Complex Programmable Logic Devices, otherwise known as CPLDs, can be used to allow host devices to support any number of SD devices. This article details a scalable, auto-sensing bi-directional multiplexer-based design.

Figure 1 shows a generalized CPLD usage model to incorporate any number of SD ports for a given host device that only

has a single native SD interface. The CPLD is placed between the host controller and the SD devices. As such, the CPLD part performs a bi-directional multiplexing function, allowing the host to communicate with any selected SD device. More importantly, this design has no directional control pins, which means that the CPLD automatically detects the direction of data flow.

This implementation is extremely flexible and scalable, meaning that the number of SD ports can be increased or decreased as desired. The design also supports any of the defined SD card modes – SPI, 1-bit, or 4-bit data modes.

While the primary purpose of using a CPLD device in this type of application is to provide additional SD ports to the host controller, secondary benefits include level translation and logic isolation between the host and the SD card. Figure 1 shows the case where the host is 1.8 V but the SD Devices are 3.3 V. The industry's latest CPLDs provide negligible standby current and ultra-low dynamic power consumption. Hence, incorporating a complex programmable logic device in your system will not significantly impact your power budget.

Compliance with the SDA Specification

The SDA (Secure Digital Association) specification states that one SD bus can only support one SD device. The clock pin can be shared, but the DAT[3:0] and CMD lines must be unique for every SD device. See Figure 2 for additional details.

This reference design is fully compliant with the SDA Specification. The following section will show you how to satisfy the above requirements while supporting any number of SD devices using a controller with a single bus.

CPLD Design

A block diagram showing typical use of this design for two SD devices sharing the same SD host interface can be seen in Figure 3. Conceptually, the design can be viewed and used as a bi-directional multiplexer. The host device controls the

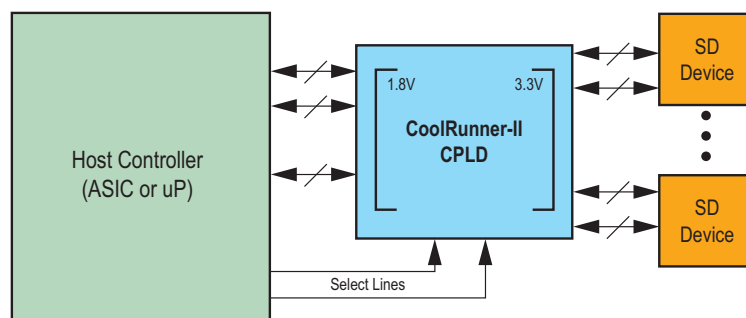


Figure 1 – Using CoolRunner-II CPLDs to provide additional SD ports

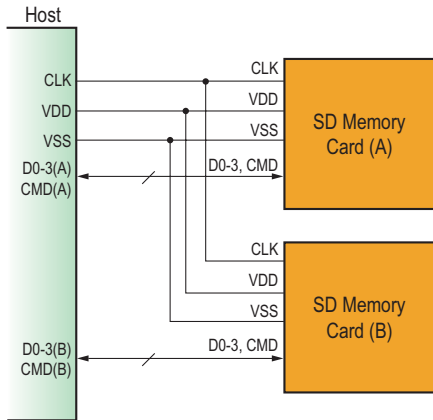


Figure 2 – SD system bus topology

CPLD via the ‘Select’ signals, thereby dictating which SD device to communicate with. Once an SD device has been selected, the logic in the CPLD device automatically detects the direction of data flow and allows data to stream accordingly (either from the host to the SD card or from the SD card to the host). A directional control pin is not required, thereby making this design easy to use.

The host can access each SD device individually without affecting the state of the other when the multiplexer is switched accordingly. If neither the host nor the SD is driving data, the CPLD allows the system to be in the default high impedance with weak pull-up state. The primary purpose of this circuit is to provide additional SD capability to the host, but this circuit can also be used to provide level translation and/or logic isolation.

Implementation Details

Figure 4 shows the actual logic circuit for a 1:2 bi-directional multiplexer design, which can be described using VHDL. In the initial condition or idle state, the Host and SD cards should be high impedance with a weak pull-up. Hence, the circuit in Figure 4 is designed to 3-state the CPLD’s output buffers, thereby allowing the external pull-up resistors to take effect. Register A (A_REG) and Register B (B_REG) are both designed to be initialized to logic ‘0’ upon power-up.

The SD cards are selected via the ‘Select’ inputs to the CPLD. When ‘Select’ is logic ‘0,’ SD1 is chosen and when ‘Select’ is logic ‘1,’ the SD1 device is chosen. For simplicity

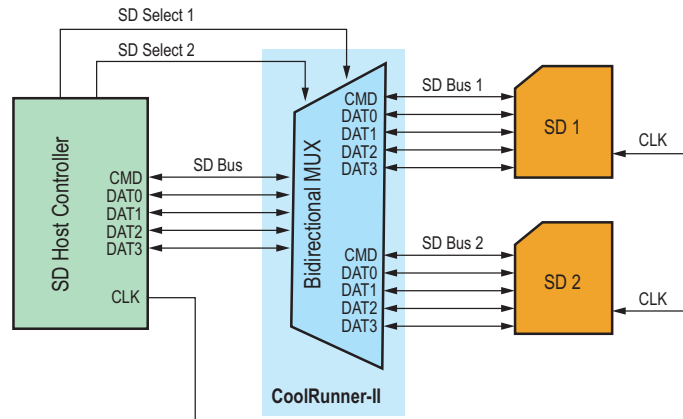


Figure 3 – Block level diagram: A bidirectional multiplexer

ty while describing this circuit, let’s assume in the following discussion that the Host is only choosing to communicate with SD1.

The auto-directional control aspect of this design is implemented in the following manner – a transaction is initiated when either the host or SD1 drives Low. For example, if the host wants to send data to the SD1 device, the host would begin by driving the A side Low. Upon driving Low, the logic in the circuit detects the Low going edge and responds by enabling the ‘B’ output buffer, but continues to keep the ‘A’ output buffer disabled. Specifically, when A is driven Low, a rising edge is delivered to

the clock input of A_REG. After clocking, A_REG’s Q output becomes logic ‘1’ and therefore prevents B_REG from receiving a clocking event. In parallel with the A_REG clocking and triggering, gate B1 outputs a logic ‘1’ when A goes Low. This enables the ‘B’ Output Buffer and, ultimately, B will follow A and drive Low.

Conversely, when it is driven from Low to High, gate B1 outputs a Low and 3-states the B output buffer. This forces B to go High via the external pull-up resistor. Once the A and B sides are both High, A_REG and B_REG are reset to 0. This process is repeated indefinitely. The reverse

 


Figure 4 – SD multiplexer circuit for two SD devices

happens when SD1 attempts to drive data toward the host. Additionally, if the host wishes to communicate with the SD2 device, the 'Select' inputs to the circuit are set to a logic '1' and the sequence of events are similar to the above.

Design Verification

Simulation Results

Functional and timing simulations have been extensively performed on this circuit using ModelSim, and test stimuli have been included with the reference design. Figure 5 shows some simulation results.

In the first part of Figure 5, the Select input is held Low. A dotted white line denotes a "Weak 1" condition, or in other words, represents a pulled-up state. In the first transaction, the host attempts to drive data toward SD1, and SD1 follows accordingly. Immediately after, the SD1 device attempts to drive data toward the host, and the host follows. Similar events happen when the Select input is driven Low. The host drives data toward the SD2 device, then the SD2 device drives data toward the host.

Hardware Results

Xilinx created an SD Multiplexer demo board, and has used this board to verify this bi-directional multiplexing design. Figure 6 shows the demo board, which features a CoolRunner™-II XC2C32A CPLD located in the center. Two SD card sockets are located along the top edge of the board. The bottom-most portion of the board is designed to mimic the physical dimensions of an SD card. Figure 7 shows the demo board plugged into a USB SD card reader. As expected, the XC2C32A allows a PC to communicate with either the first or second SD card flawlessly.

Device Utilization

Table 1 shows device utilization statistics for various implementations. As stated in the SDA specification, there are three signaling modes defined for SD cards: SPI Mode, 1-bit SD Data Transfer Mode, and 4-bit SD Data Transfer Mode. This design can be easily adapted for any chosen mode. The design can also accommodate any number of SD expansion ports, with default VHDL code set to two ports.



Figure 5 – Simulation results

Voltage and Current Considerations

The SDA specification contains stringent voltage and current requirements for SD cards. Programmable logic devices are ideal for this application because they are extremely low power and have features such as I/O Banking. The I/Os can be configured as 1.5 V, 1.8 V, 2.5 V, or 3.3 V, allowing them to interface to any SD device. CPLDs also contain I/O Banks, which allow for voltage translation capabilities between the processor and SD card.

The extremely low power nature of modern complex programmable logic devices allow for standby operation as low as 15 µA. The addition of a low power CPLD in a system will minimally impact the current budget.

VHDL Download

The VHDL files to compile and simulate these designs are located at: www.xilinx.com/products/silicon_solutions/cplds/resources/coolvhdlq.htm.

Conclusion

As SD devices gain in popularity, the need will increase for ways to support more than one SD device with host controllers. This article provides a verified solution to the problem at hand. This solution will give designers the flexibility to implement two or more SD devices into a system.



Figure 6 – Xilinx SD multiplexer demo board



Figure 7 – Xilinx demo board plugged into a USB SD card reader

Number of SD Expansion Ports	Device	Macrocell Utilization (SPI or 1-Bit Data Mode)	Macrocell Utilization (4-Bit Data Transfer Mode)
1	XC2C32A	13 Macrocells	19 Macrocells
2	XC2C32A	21 Macrocells	30 Macrocells
3	XC2C64A	27 Macrocells	39 Macrocells

Table 1 – Device utilization statistics for various implementations